

Chapter 1 - Transistors and ALU

We have heard of binary before - it is a stream of 0s and 1s - and we all know that this is the language that computers understand. But why specifically 1s and 0s? Why not 0, 1 and 2? Or 0, 1, 2 and 3? Or any other combination? This is due to the nature of the component that makes up the computer - the transistor.

The transistor is the building block of every electronic component in the world right now and the world would be very different if not for them. The structure of the transistor is as below:



It basically functions as a switch. There is always a flow of current in the top side labelled E, which is flowing downwards towards C (as labelled by the arrow). However, this current will not pass through to C unless a current is applied to B. So C can be thought of as the output and B as the input and this output can have two states:

- Current flowing through it (represented as 1)
- No current flowing through it (represented as 0)

And this is the reason why we represent everything with either 0 (transistor off) or 1 (transistor on). The transistor might seem trivial and it is on its own - but combining billions of these results in machines that can do some pretty complex operations like the phones and laptops we all use.

However, we can't just accept this - everyone says transistors are the building blocks, but until we see for ourselves, we shouldn't accept it, which is why this


project exists. We will be building a simple version of one of the most important components in today's world - the CPU - and we will build it from the ground up, that is by understanding everything from the transistor level so we can see for ourselves how transistors work together. First we can start by looking at logic gates from a transistor level.

Logic Gates

Logic gates are the building blocks of digital circuits. They perform Boolean operations on one or more binary inputs (0 or 1) to produce a single binary output. There are four main gates we will be looking at, starting with the AND gate.

AND Gate

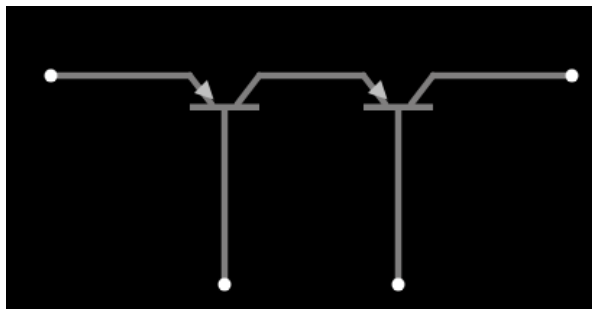This is simply achieved by placing two transistors in series as below




A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

As always, the current to the two bases are the inputs and the node at the very right is the output. The output would only be high if both inputs are high and this models an AND gate.


Simply changing this arrangement can help us model other gates as below (as always rightmost node is the output and anything to the base is the input):

OR Gate

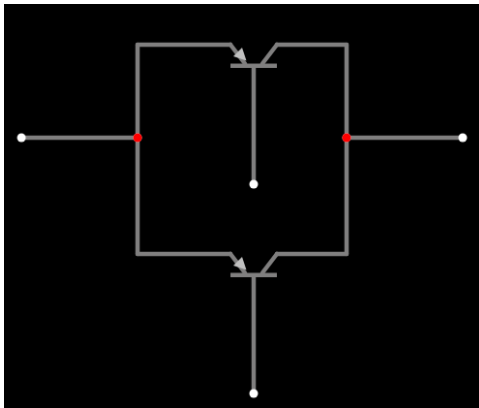



A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

NOT Gate

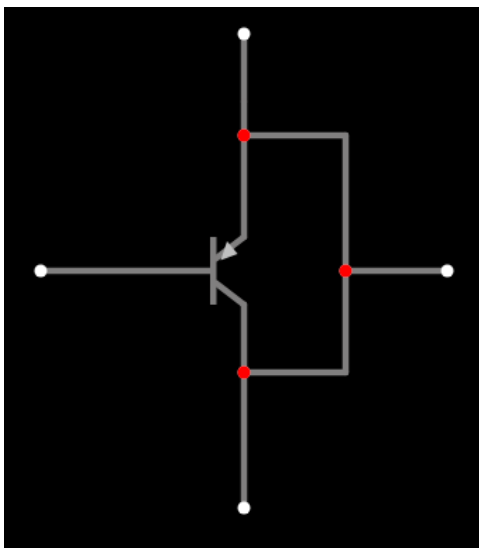

A	B
0	1
1	0

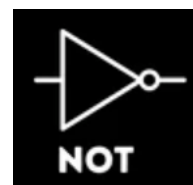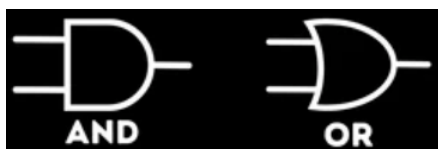These three gates can be used to make any logic circuit we desire, which is why from now we will assign symbols to each of them and the rest of the gates will build on these symbols - if not the design may seem too big and intimidating.



Other common gates like the XOR, NAND and NOR gate can be modelled using the above. A NAND gate is simply an AND gate followed by a NOT gate, whereas a NOR gate is simply an OR gate followed by a NOT gate. An XOR gate is slightly more complex and be built as below:


A	B	Output
0	0	0
1	0	1
0	1	1
1	1	0

Now that we know the basic gates, we can start building more complex components with these gates - lets start with some simple mathematical operators - the adders.

Half Adder and Full Adder

There are two types of adders - half and full. Why are they named this way? Well, to understand that let's look at the structure of these two.

Half Adder

 


A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

As we can see above, the half adder takes in two inputs, A and B, and returns two outputs, sum and carry. The truth table is above and the functioning is pretty self explanatory. But this only performs calculations on two bits - what if we wanted to perform addition on multiple bits? This would require us to connect multiple half adders together but the problem is that the carry from each half adder would be ignored as the half adder only has two inputs so we are limited.


This is the reason they are called **half** adders. Full adders, as you might've guessed take in three inputs - A, B and Carry in, and therefore are more suited for many more operations.

Full Adder

 


Full Adder				
A	B	C	C Out	Sum
0	0	0	0	0
1	0	0	0	1
0	1	0	0	1
1	1	0	1	0
0	0	1	0	1
1	0	1	1	0
0	1	1	1	0
1	1	1	1	1

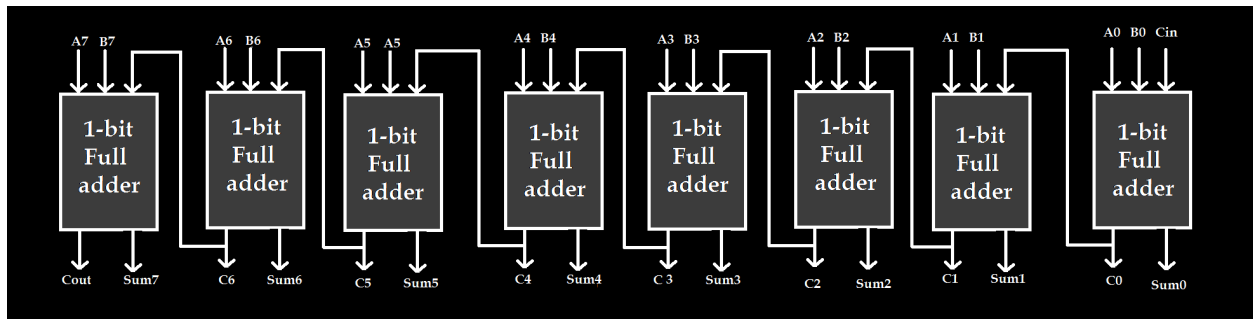The structure of the full adder is as above. It takes in a carry in addition to A and B and returns both the sum and carry out. This is much more useful as they can be cascaded to form multiple bit adders. A common use case is a 8 bit adder, which looks like this and would be the first component of our ALU.



This would take in two 8 bit binary numbers and output the sum, along with an overflow. If we keep one 8 bit binary number as 1 always, this can easily be made into an incrementer.

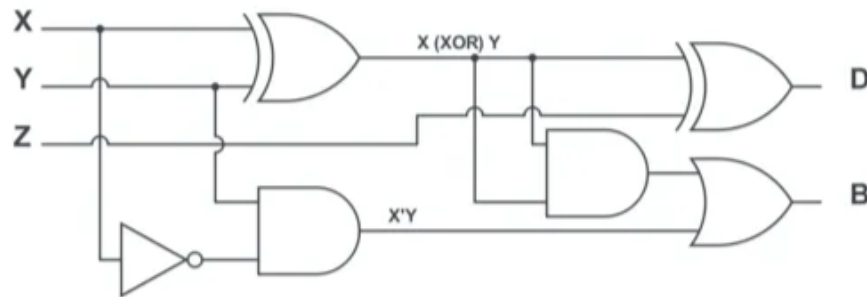
In the same way, lets look at a structure of a full subtractor



This can be combined in the same way as before to form an 8 bit subtractor and consequently an 8 bit decrementer as well. This leaves us with four components:


- 8 bit adder
- 8 bit subtractor
- 8 bit incrementor
- 8 bit decrementer

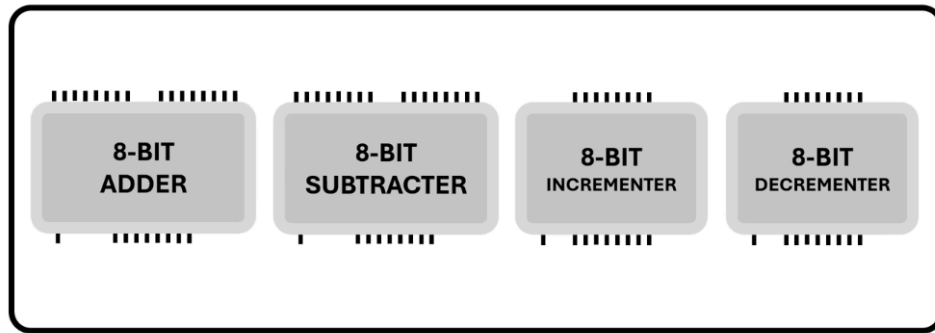We can build a very simple ALU with these components.




But how does the ALU know which component should the output value of an instruction come from? If you have two 8 bit numbers as input that you want to add, you can't take the output of all components - it should be the output of just the adder. But how can we tell the ALU this? This is where opcodes come in. These are instructions that tell the ALU to add, subtract, increment etc and this is what the ALU receives in binary format.

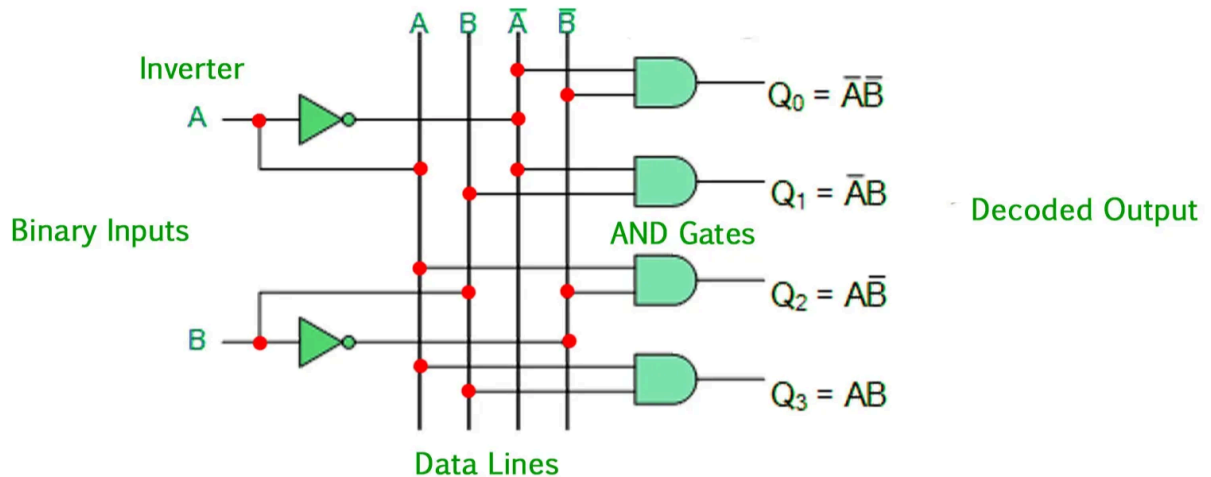
This opcode in binary format can be sent through a decoder to only choose one component to 'activate'. The structure of the decoder is as below:



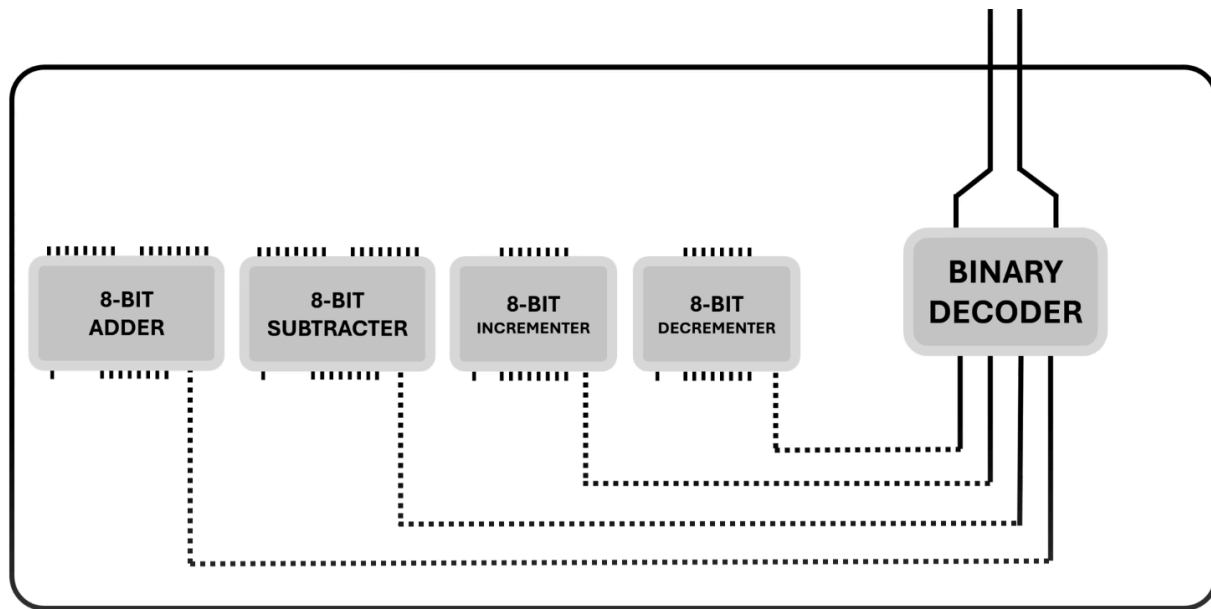As we can see above, only one of the outputs will be high at each combination of A and B. This is perfect for what we need and we can integrate it into the ALU as below:



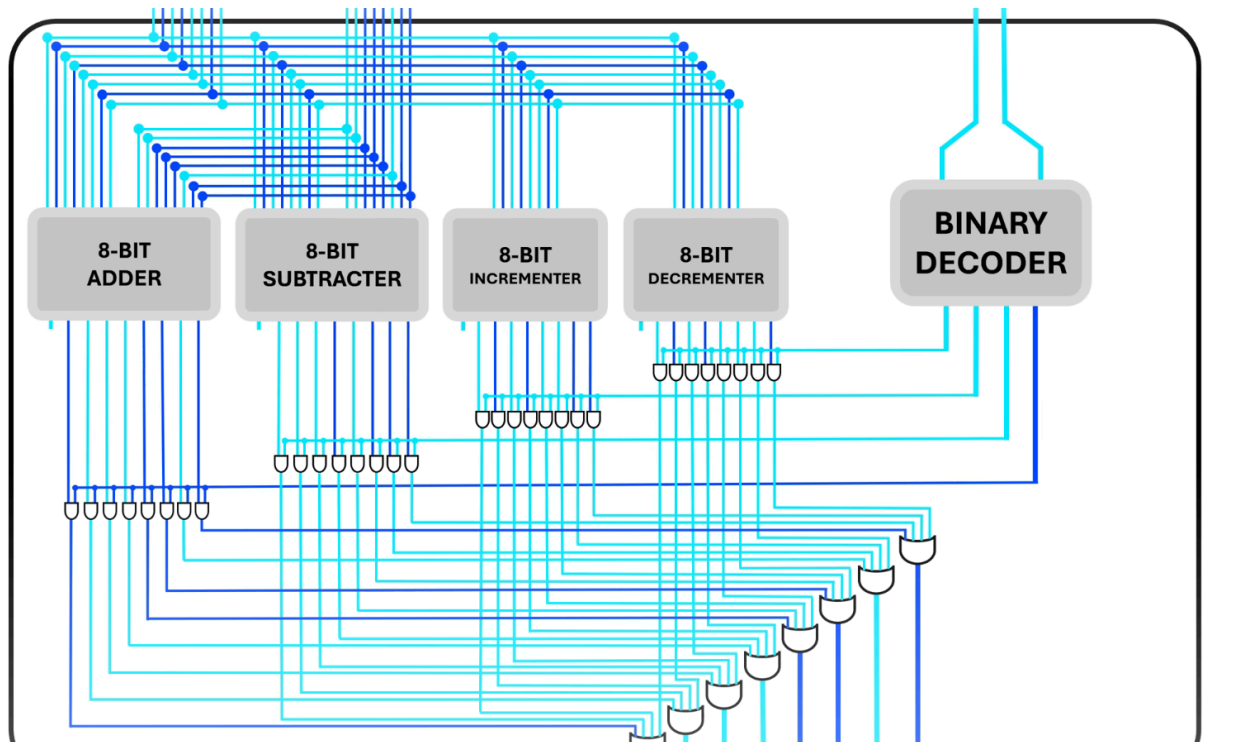What exactly is this binary decoder connected to tho? We said that we can 'activate' one component but that's not exactly true. The way the decoder works is by choosing which of the outputs is sent through by using an enable. All components are fed in the 8 bit values and output one 8 bit value each, but the decoder decides which of these outputs are sent through by using an enable as seen below.



This sums up a very simple version of the ALU.

